

Remember...

1. turn projector off
2. do NOT look tables
3. push chairs in


4/7 ①

example P193.

Question: what's this configuration?

Memory bank design
The objective of the memory bank design is to integrate multiple memory chips into one system and meet the system requirement.

Address space of the memory bank

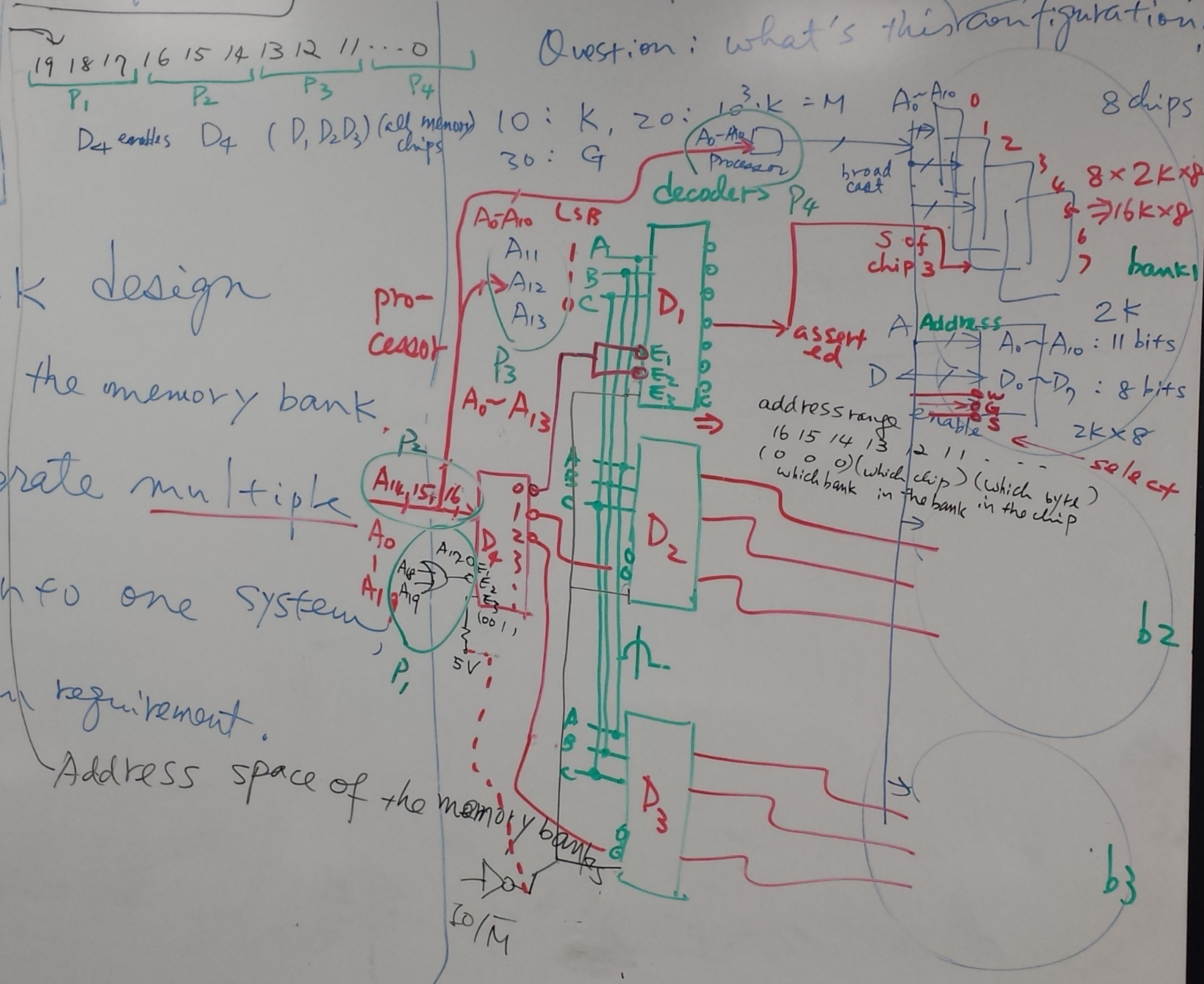

when $(19, 18, 17) = (000)$,
 D_4 enabled, it will assert one
output based on the input value
 the input: $(16, 15, 14)$

each output corresponds to
 one bank: $\{8 \text{ chips}\}$

• For the chosen decoder, say D_2 ,
 it asserts the output corresponding
 to its inputs $(13, 12, 11)$.

each output
 corresponds to
 one chip in
 a particular bank

• The asserted output enables its connected
 chip, in


• $A_0 - A_{10}$ broadcast to all chips

• Data lines all "tied" together

⇒ only the asserted chip will set values on D lines


$A_0 - A_{10}$, some junior engineer
 made a mistake. swap 2 lines

$A_{11}, A_{10} \dots A_0$

 

Q ⇒ what would happen? can a software test
 detect the error?

What if this happens to inputs
 D_4 ?

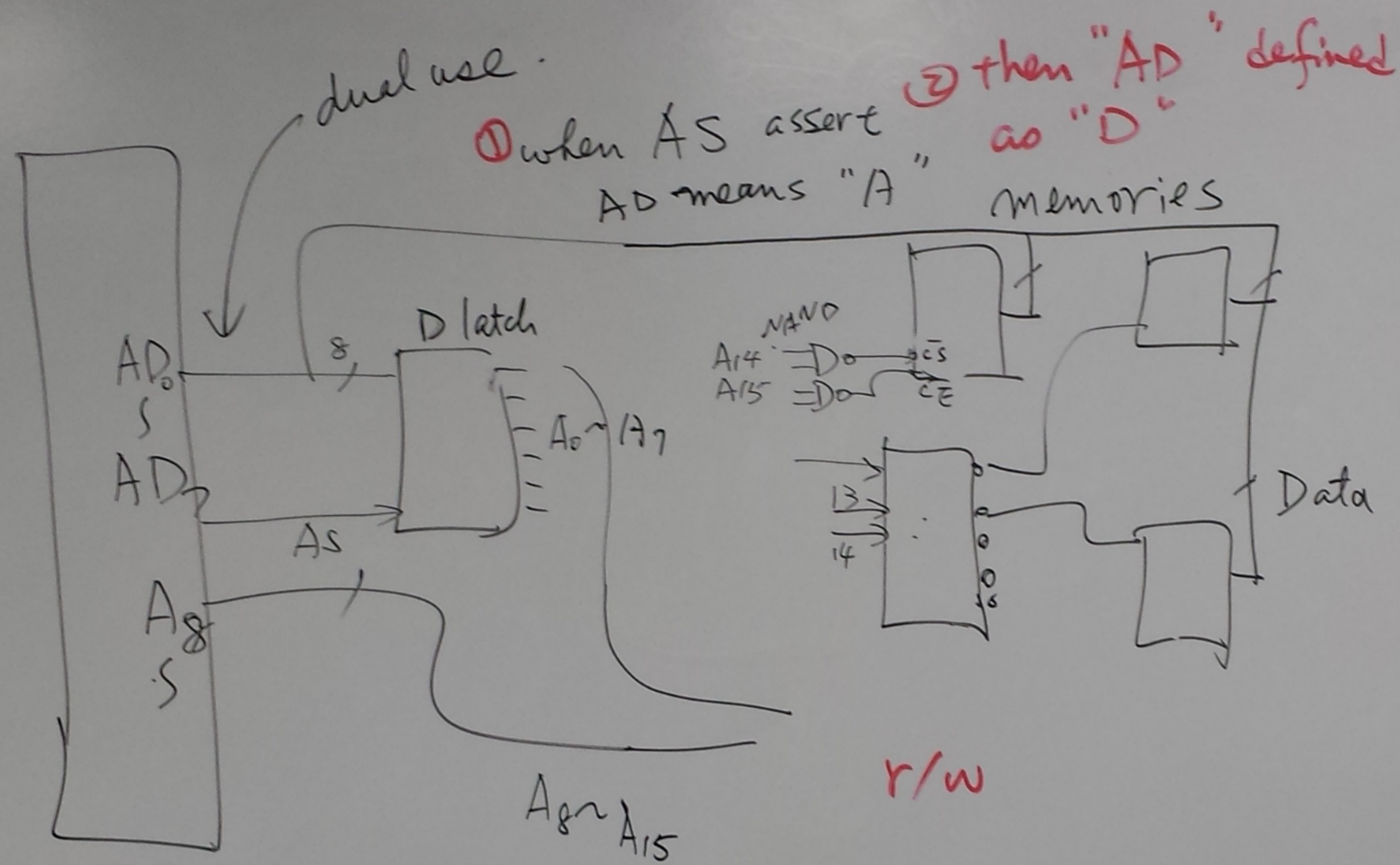

What's the address space
 distribution?